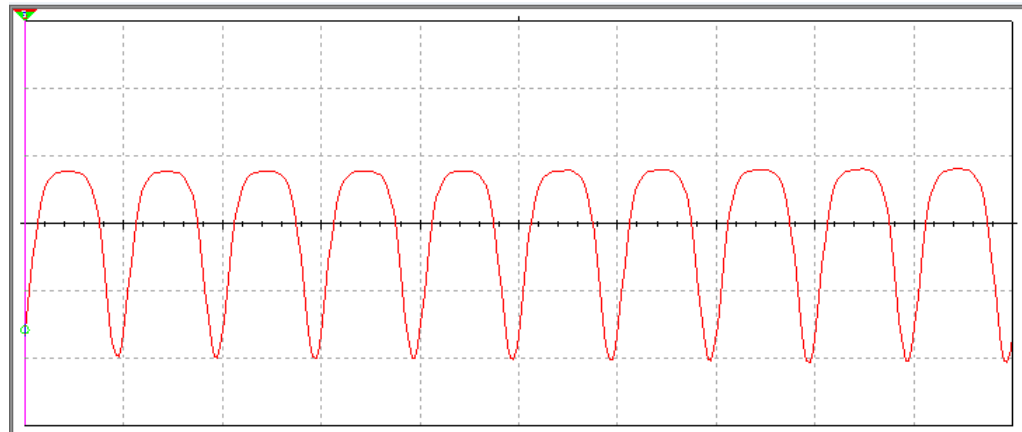


基本放大电路	U_s	U_i	U_o	U_L	A_u	R_i	R_o
	1.154mv	1.1mv	1.307v	0.642v	1300	10k Ω	1k Ω
其中测量输入输出电阻的时候，R均选择1k Ω							

负反馈放大电路	U_s	U_i	U_o	U_L	A_u	R_i	R_o
	10mv	9.539mv	0.953v	0.929v	95	20k Ω	25.8 Ω
其中测量输入输出电阻的时候，R均选择1k Ω							

基本放大器	f_l (kHz)	f_H (kHz)	Δf (kHz)
	0.258	21	20
负反馈放大器	f_{lf} (kHz)	f_{Hf} (kHz)	Δf_f (kHz)
	0.027	641	641

	$U_{CQ1}(V)$	$U_{BQ1}(V)$	$U_{EQ1}(V)$	$UCE(V)$
实测值	7.5	3.57	2.43	5.07
	$U_{CQ2}(V)$	$U_{BQ2}(V)$	$U_{EQ2}(V)$	$UCE(V)$
实测值	7.45	3.23	2.64	4.22



示波器-XSC3

